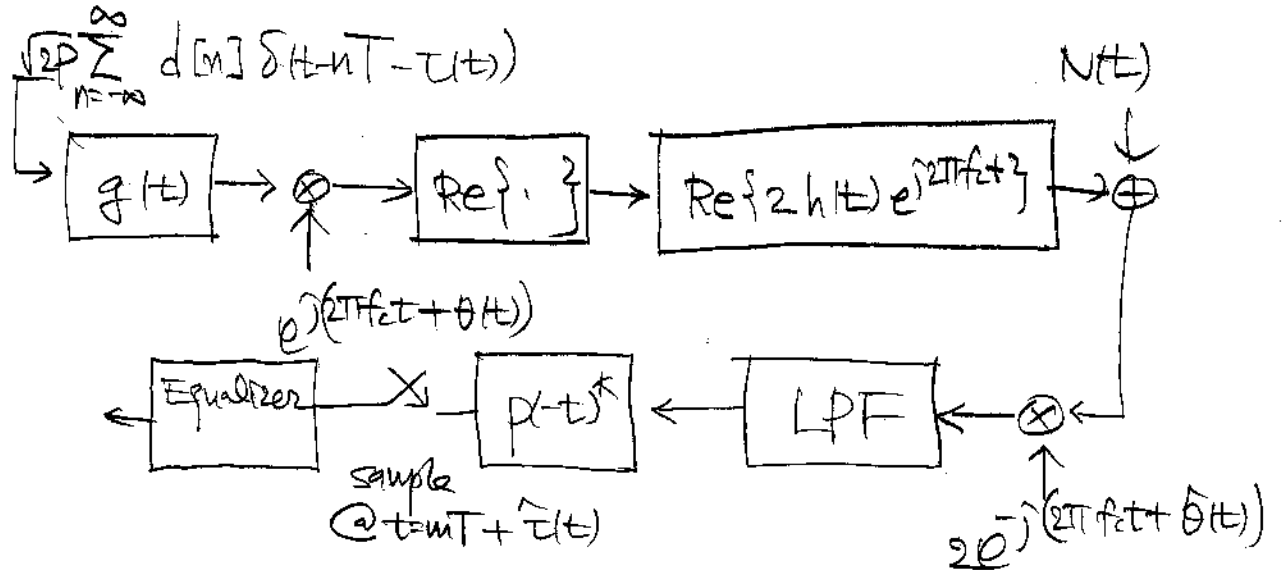


Synchronization

(Based on J.M. Coffe, Digital Communications, Chapter 6 & Barry, Lee, Messersmith, Digital Communication, 3rd ed. chapters 14-16)

Assumptions made so far

- block diagram



Assumptions in Tx

- (i) The source **message clock** is synchronized to the symbol clock.
- (ii) The **symbol clock** and **carrier frequency** are locked.
- (iii) $\tau(t) = \text{constant}, \forall t, \theta(t) = \text{constant}, \forall t.$

Assumption in Rx

- (i) $\hat{\theta}(t) = \theta(t), \forall t, \hat{\tau}(t) = \tau(t), \forall t.$


Assumption in Channel

- (i) The channel is well modeled by an LTI system.


Realities

- Often, **pilot or training signals**, ^{symbols, or tones} are embedded in the transmitted signal.

Two main approaches for tracking

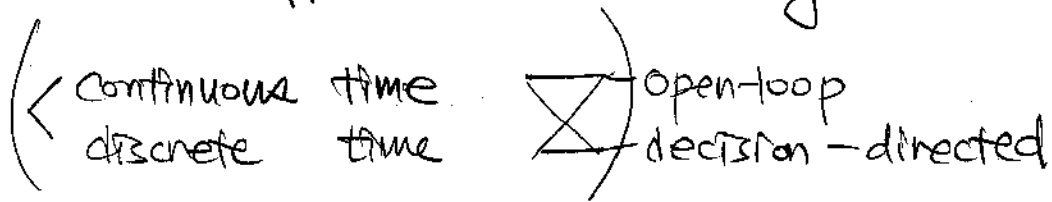

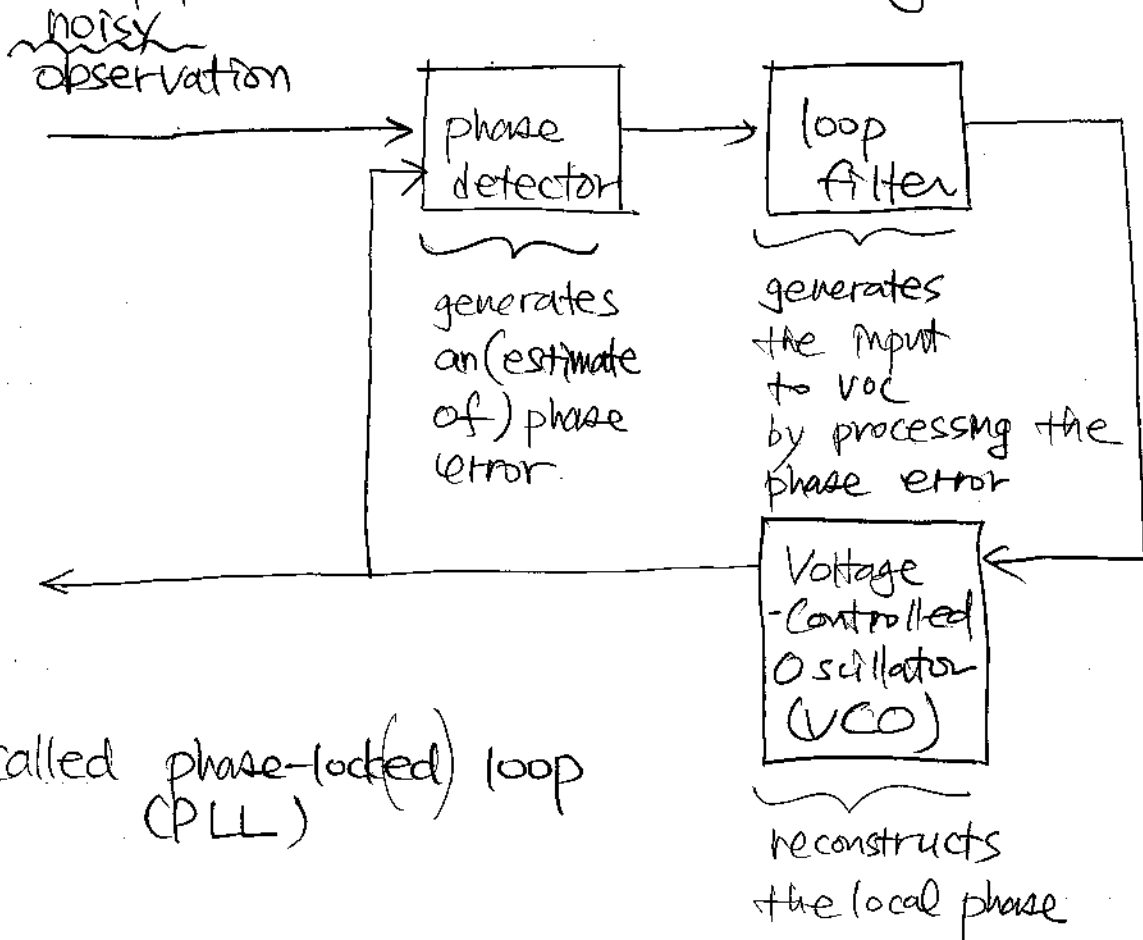Most popular structure for tracking phase angle.



called phase-locked (PLL) loop


If reduce the delay in loop filter, then vulnerable to noise,

→ trade-off!

• why PLL?

The PLL underlies most synchronization techniques.

o PLL

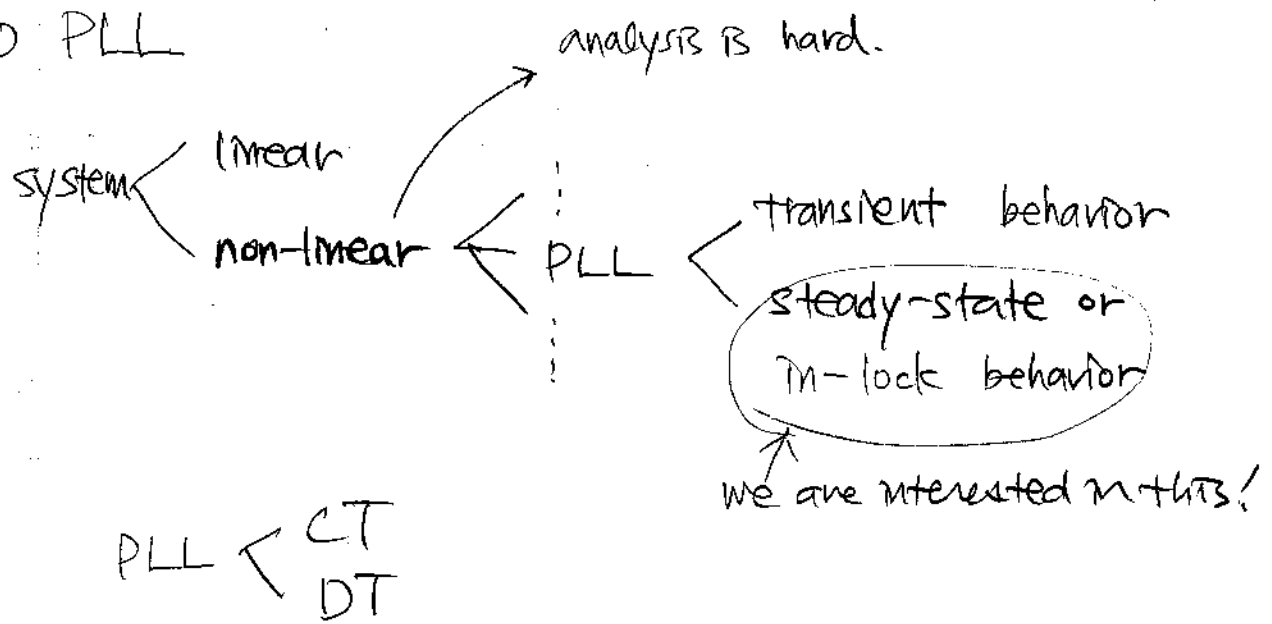


o CT PLL

mainly based on
(BLM, Digital Commun. Ch. 4.1)

- Assumptions

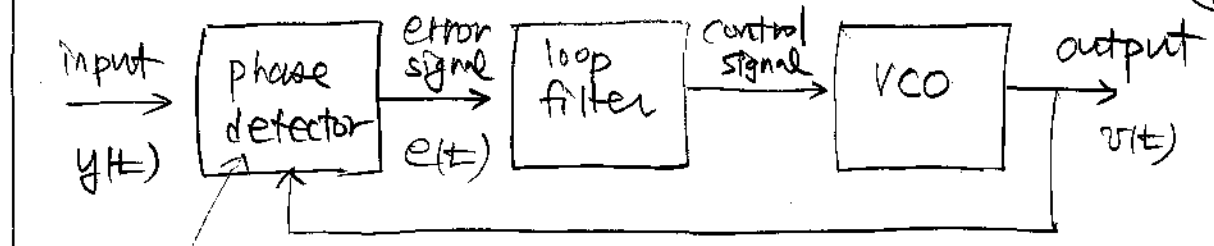Input : $y(t) = A_y \cos(\omega_c t + \theta(t)) + \text{noise}$
 Even if the freq. of input is not ω_c , we can write in this form



VCO output : $v(t) = A_v \cos(\omega_c t + \hat{\theta}(t))$


nominal free-running frequency of the VCO.

- phase detector

any gain is included in the loop filter.

Output of ideal phase detector : $e(t) = \theta(t) - \hat{\theta}(t)$


Sawtooth modulo -2π phase detector:

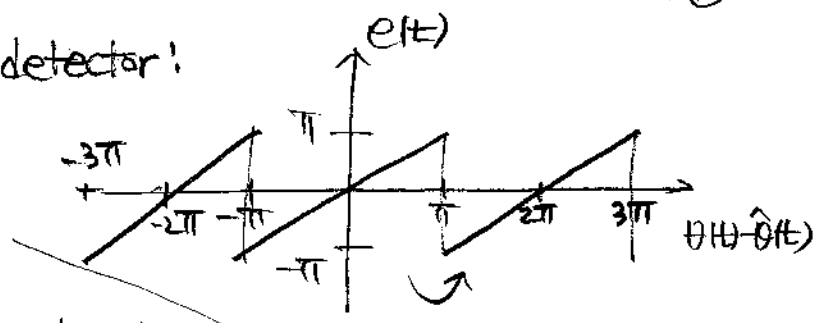

Maximum Likelihood phase estimator: a series of approximations

cycle slip occurs, leading to a quantity of phase error.

demodulating phase detector:

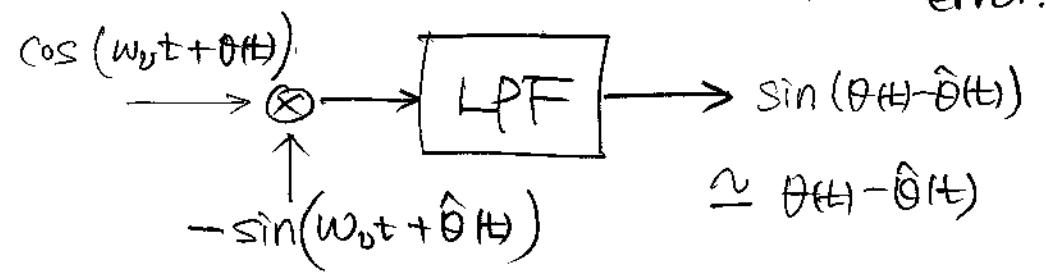


$$-\sin(w_c t + \hat{\theta}(t)) \cos(w_c t + \theta(t))$$


$$= -\sin(2w_c t + \hat{\theta}(t) + \theta(t)) + \sin(\theta(t) - \hat{\theta}(t))$$

sampling phase detector:

binary phase detector:

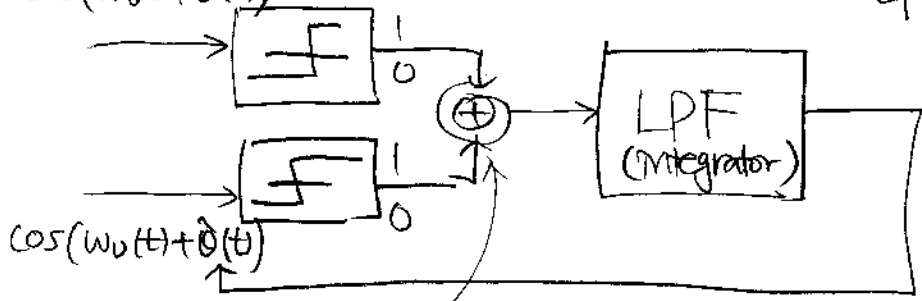

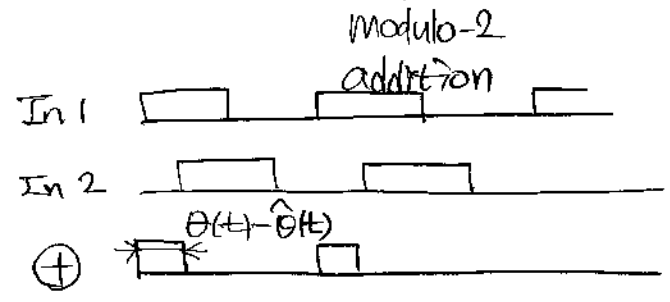$\cos(w_c t + \theta(t))$ \times LPF
@ rising edge of $\cos(w_c t + \hat{\theta}(t))$



- VCO

- ideal VCO: output $v(t) = A_D \cos(\omega_0 t + \hat{\theta}(t))$

$$\frac{d\hat{\theta}(t)}{dt} = K_{VCO} \cdot e(t) \quad \dots (*)$$

Analog VCO physics is beyond the scope.

input = output of phase detector

- loop filter

1st order PLL has the loop filter that has

$$L(s) = K_L$$

2nd order PLL has " " " " " "

$$L(s) = K_L \left(\frac{s + K_1}{s + K_2} \right) \text{ or}$$

$$= \alpha + \frac{\beta}{s}$$

Note that, by (*), $\dot{\hat{\theta}}(t) = K_{VCO} \cdot L(t) * e(t)$

$$\Rightarrow \frac{\hat{\theta}(s)}{\theta(s)} = \frac{K_{VCO} \cdot L(s)}{s + (K_{VCO} \cdot L(s))}$$

[A PLL is phase locked if $\theta(t) - \hat{\theta}(t) = \text{const.}$
" " " perfectly phase locked if " = 0.

- The 1st order PLL may not be perfectly locked.
- α & β must be chosen to make phase locked (perfectly.)
- Analysis of 1st-order & 2nd-order PLL is

omitted here. See references

o DT PLL

Similar to CT PLL except that we need to use z-transform instead of Laplace transform